



A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

(1)

A	B	Output
0	0	0
0	1	0
1	0	1
1	1	0

(2)






A	B	Output
0	0	0
0	1	1
1	0	0
1	1	0

(3)


A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

(4)

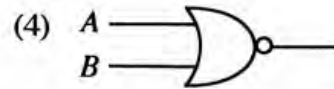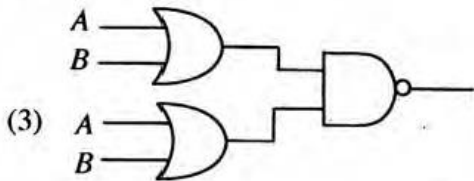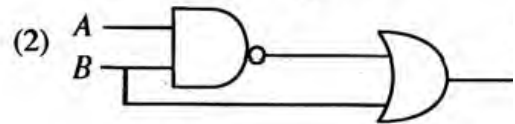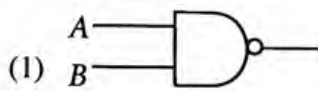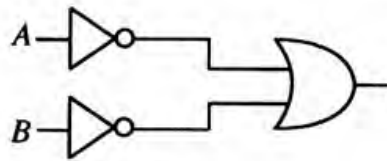6. Which of the following logic circuits has a truth table equivalent to the truth table of the logic circuit shown on the right hand side? (2017)






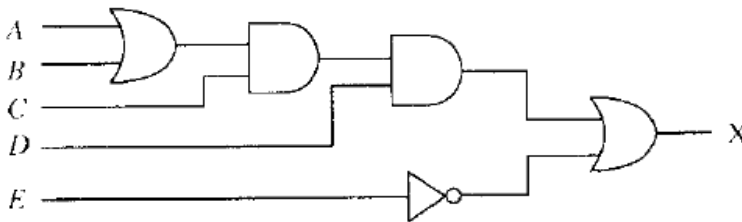7. Consider the following logic circuit. (2018)



Which of the following is equivalent to the above circuit?

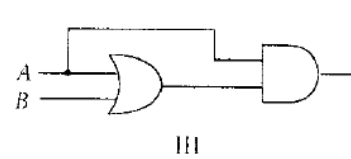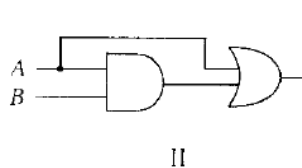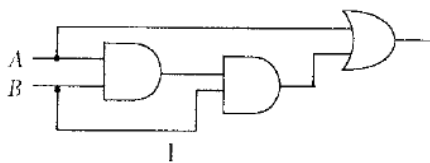
- 1)  $X = (A + B) \cdot C \cdot (D + \bar{E})$   
 2)  $X = (A + B) \cdot C \cdot D + \bar{E}$   
 3)  $X = (A \cdot B) + C + D \cdot \bar{E}$   
 4)  $X = (A + B) \cdot (C + D) + E$
8. For given inputs, which of the following logic circuits provide the same output? (2018)



- 1) I and II only  
 2) I and III only  
 3) II and III only  
 4) All I, II and III


9. If 0 and 1 respectively are given as inputs for X in the following logic circuit, what would be the two respective outputs at Y? (2019)

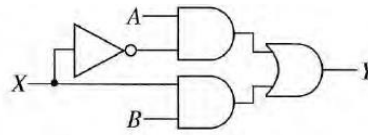- 1) A,  $\bar{B}$
- 2) A, B
- 3) B,  $\bar{A}$
- 4) B, A




10. Which of the following Boolean expression is equivalent to the output of the given logic circuit? (2020)


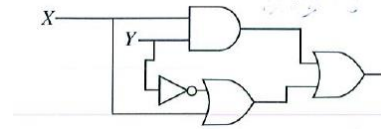
- 1)  $(X \cdot Y) + (\bar{Y} + X)$
- 2)  $(X + Y) \cdot (\bar{Y} \cdot X)$
- 3)  $(X + Y) \cdot (X \cdot \bar{Y})$
- 4)  $(X \cdot Y) + (Y + \bar{X})$



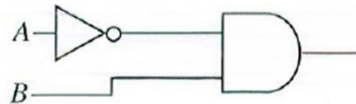11. Consider the following logic circuit: (2020)



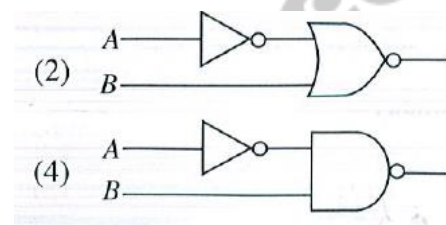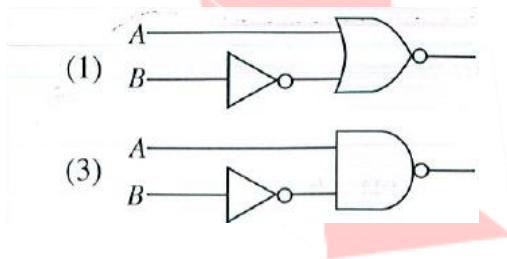Which of the following logic circuits has a truth table equivalent to the above logic circuit?



Lakshmanrushi.com